

# Design of Digital Circuits

## Sequential Circuits

...

Michiliia Gureva

Sandeep Kumar

Stephen Nnamani

Vulcu Horia - Rares

Yew Heng Ngoh

# Overview

1. D-Flip-Flop
2. JK-Flip-Flop
3. Sequence Detector
4. Shift Register
5. Serial Adder

# 1. D-Flip-Flop

## Synchronous SR- Latch to D-flip-flop:

- The SR-Latch is in Active High, which means irrespective of the clock cycle if Q was once High it will remain will remain high until the reset R input goes high.


8 of 8 rows shown

S	Clk	R	Q	Qn
0	0	0		
0	0	1		
0	1	0		
0	1	1	0	1
1	0	0		
1	0	1		
1	1	0	1	0
1	1	1	1	1

Reset


Set

Invalid

 

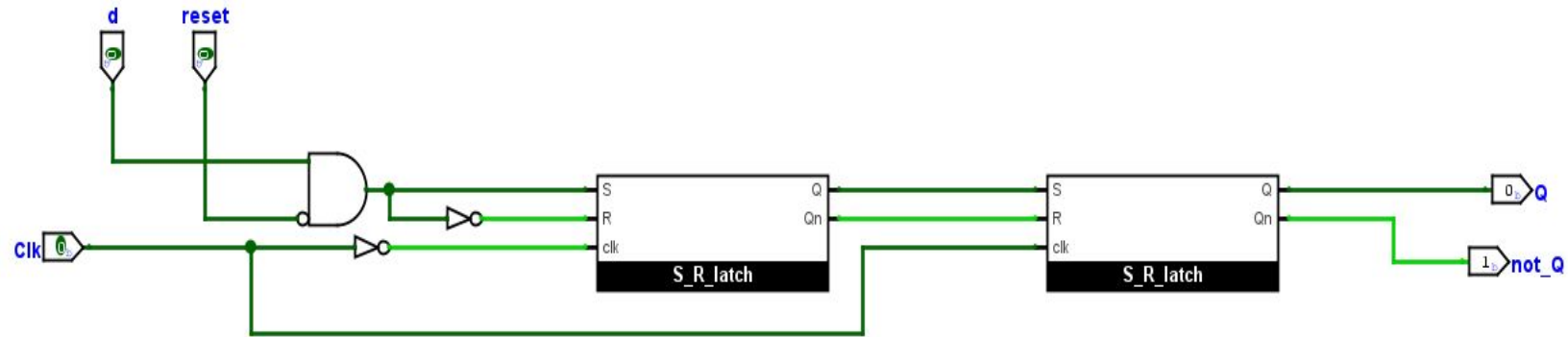
## Positive Edge Triggered D-flip-flop with Synchronous reset:

- A D flip-flop with synchronous reset, the reset signal is synchronized with the clock signal.
- The flip-flop only resets when both the clock signal and the reset are high at the same time.




 
## Chronogram for D-Flip-Flop:

The initial Error is due to the recursive Q and not\_Q which were connected to the internal Signal-loop. I overcame this by just putting toggling the clock my low to high.




## 2. JK-Flip-Flop

  

# 3. Sequence Detector

1. Finite state Machine state Diagram:

 

Mealy Machine  
Sequence 1: 00;01;11  
Sequence 2: 00;11

2. State encoding:



A = 00

B = 01

C = 10

### 3.State transition table & optimized input equations:

Index	Input		Current state		Next State		Z		
i	X <sub>0</sub>	X <sub>1</sub>	State	Q <sub>1</sub>	Q <sub>0</sub>	State	Q <sub>n</sub>	Q <sub>n+1</sub>	Output
0	0	0	A	0	0	B	0	1	0
1	0	1	A	0	0	A	0	0	0
2	1	0	A	0	0	A	0	0	0
3	1	1	A	0	0	A	0	0	0
4	0	0	B	0	1	B	0	1	0
5	0	1	B	0	1	C	1	0	0
6	1	0	B	0	1	A	0	0	0
7	1	1	B	0	1	A	0	0	1
8	0	0	C	1	0	B	0	1	0
9	0	1	C	1	0	A	0	0	0
10	1	0	C	1	0	A	0	0	0
11	1	1	C	1	0	A	0	0	1
12	0	0	D	1	1	X	X	X	X
13	0	1	D	1	1	X	X	X	X
14	1	0	D	1	1	X	X	X	X
15	1	1	D	1	1	X	X	X	X

 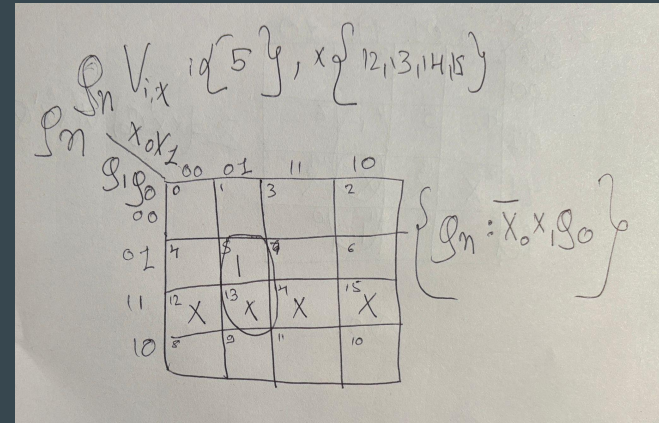




$Z_1: i: \{7, 11\}, X: \{12, 13, 14, 15\}$

$Z = \sum x^0 x^1 g_0 + \sum x^0 x^1 g_1$


	$x^0$	$x^1$	
$g_0$	00	01	11
00			
01	7	5	6
11	12	13	14
10	8	9	10

$$Z = \sum x^0 x^1 g_0 + \sum x^0 x^1 g_1$$

#### 4. circuit in Logisim:

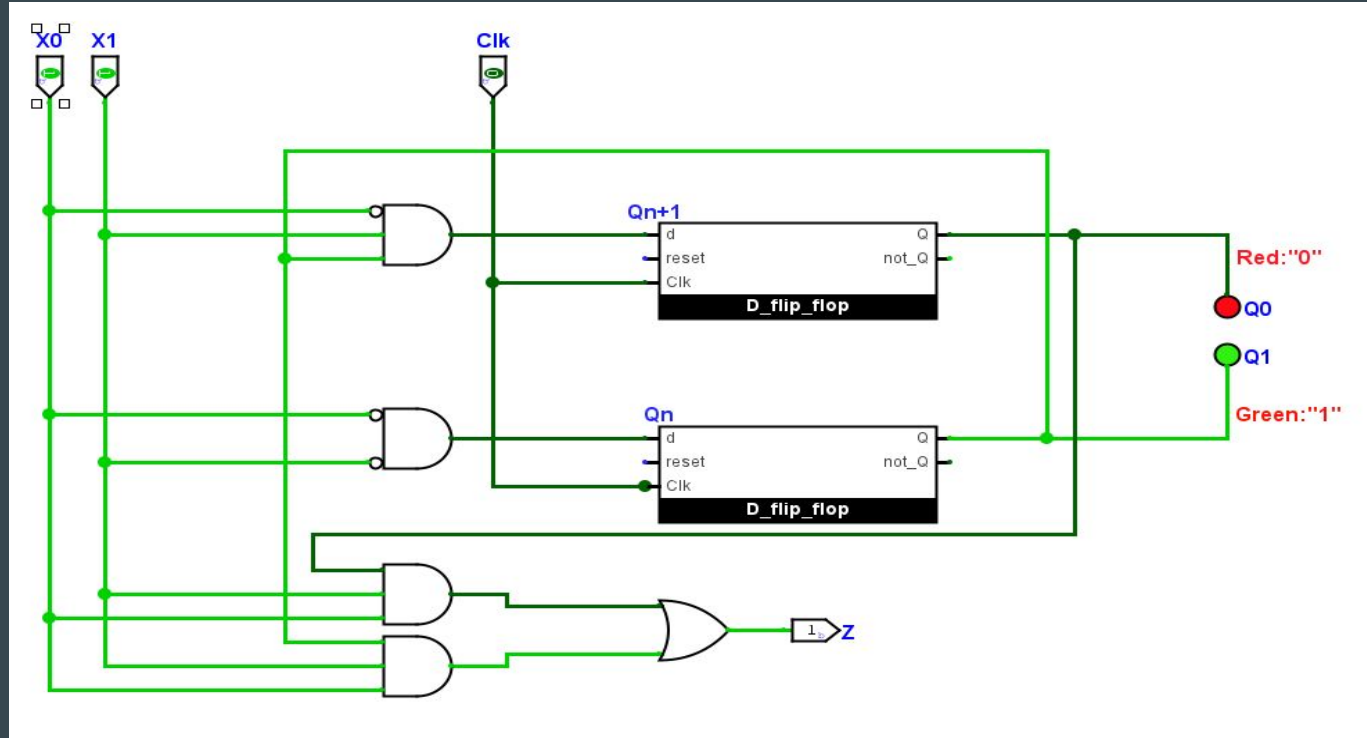


## 5.Chronogram

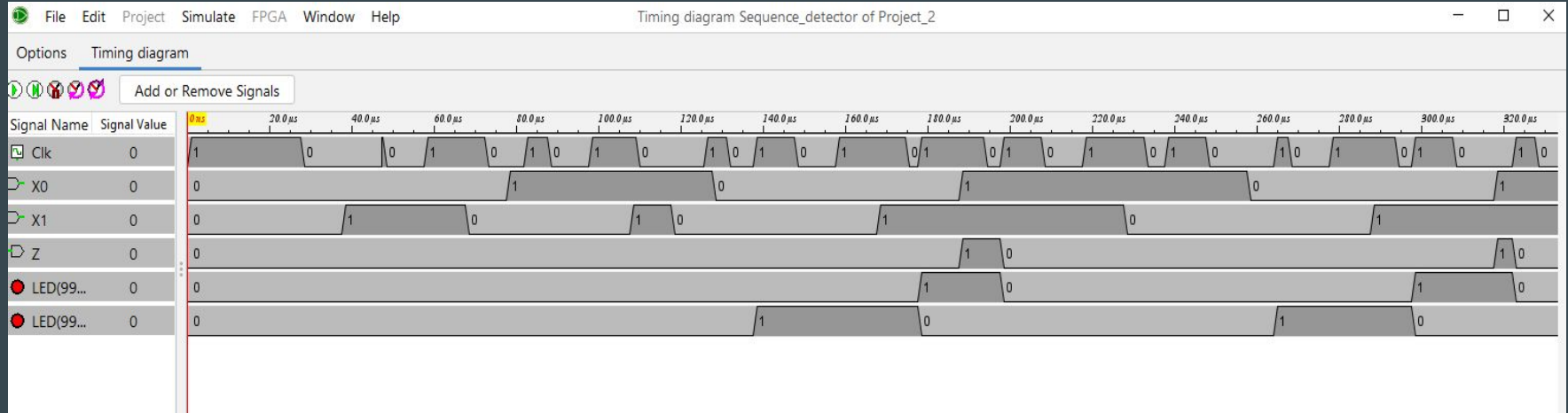


# 4. Shift Register

3 to 1 Multiplexer

 


# 4. Shift Register

## 1-bit Shift Register

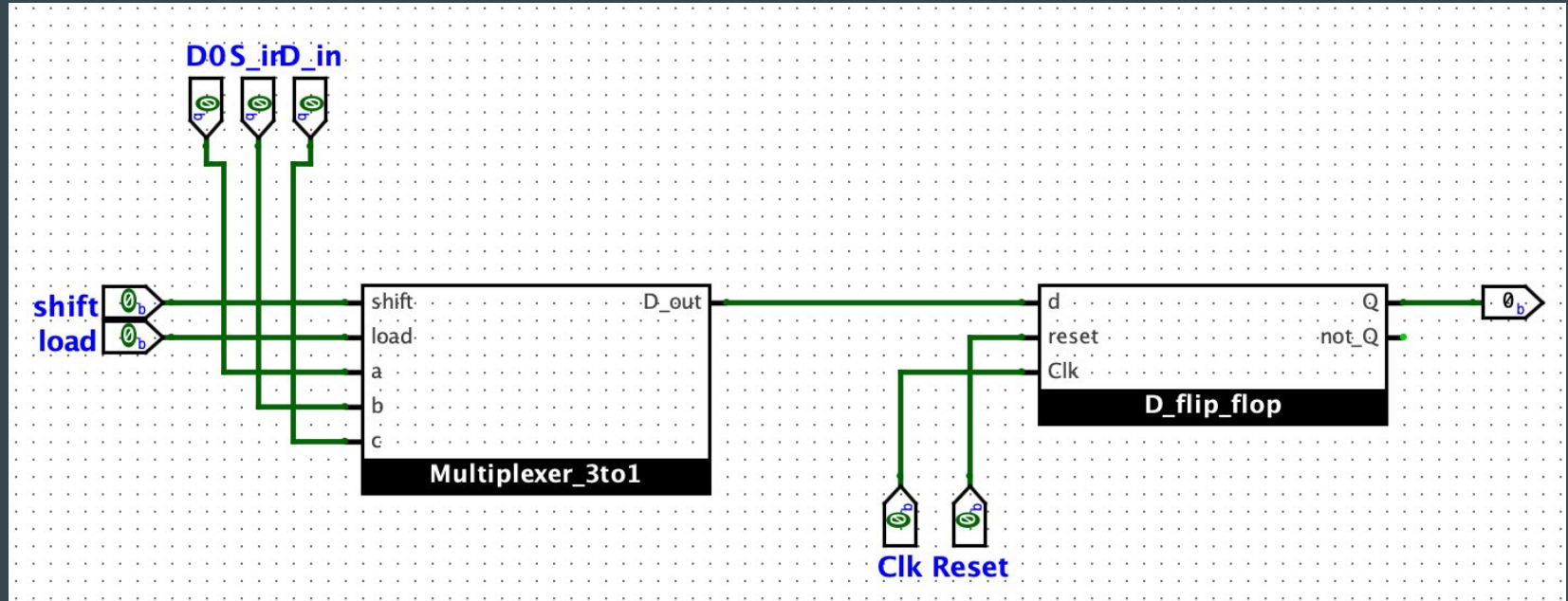


# 4. Shift Register

4-bit Shift register

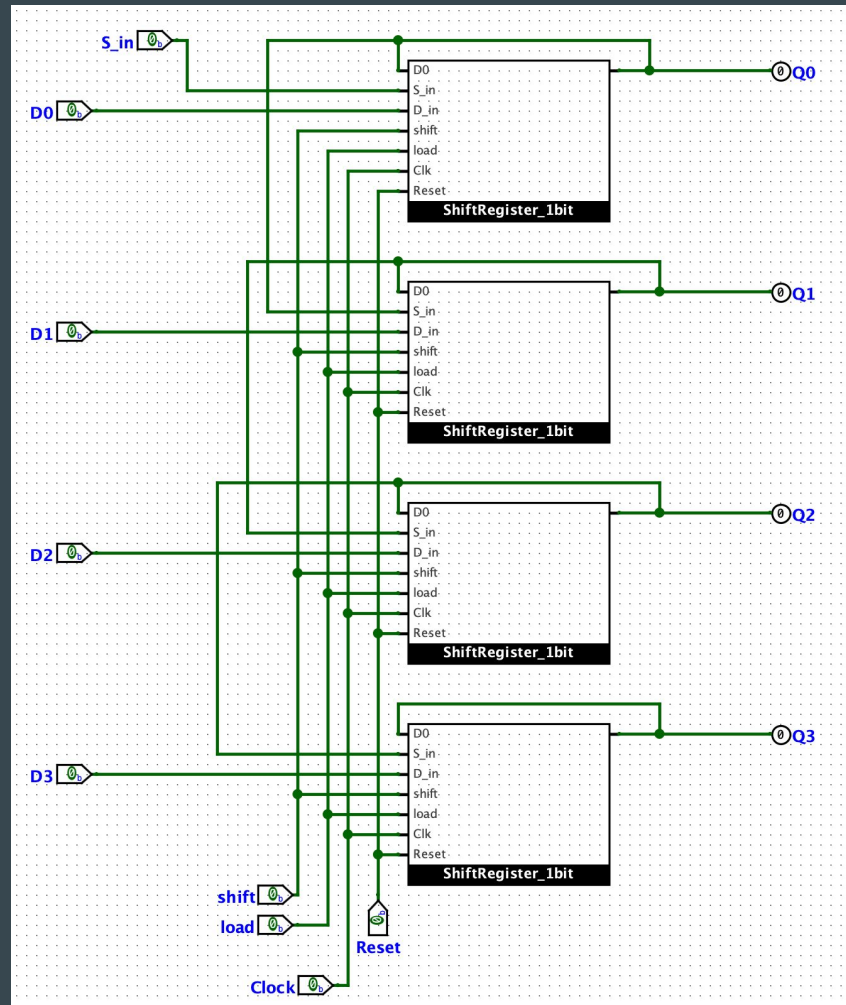

# 5. Serial Adder

Pen & paper test

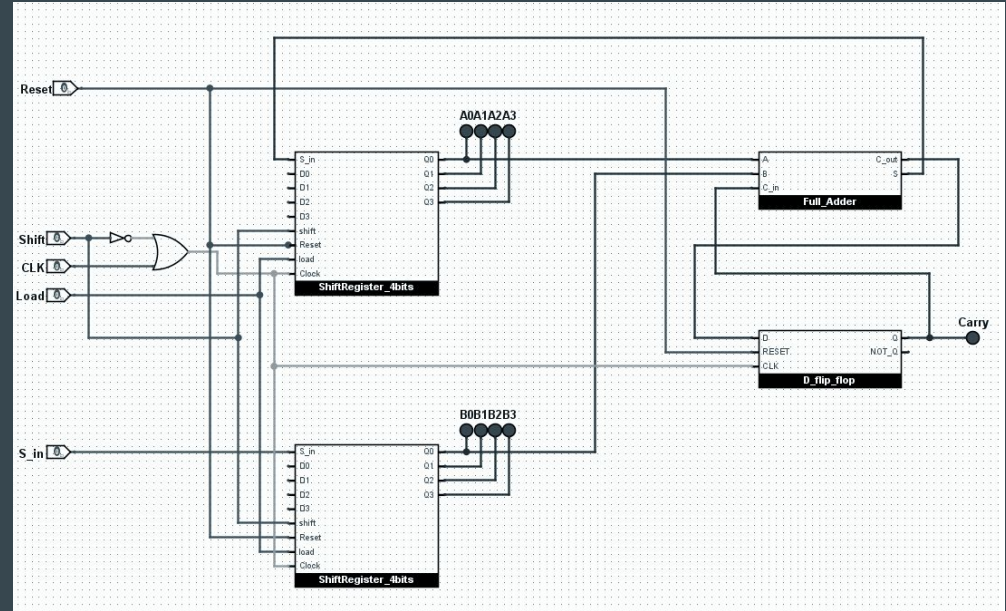

	Tick 0	Tick 1	Tick 2	Tick 3	Tick 4	Tick 5	Tick 6	Tick 7	Tick 8	Tick 9	Tick 10	Tick 11
Register A	0000	0000	0000	0000	0000	1000	1100	0110	0011	0001	0000	0000
Register B	0000	1000	1100	0110	0011	1001	0100	1010	0101	0010	0001	0000
Carry	0	0	0	0	0	0	0	0	0	1	1	1
Sum	0	0	0	0	1	1	0	0	0	0	0	0
Sin	1	1	0	0	1	0	1	0	0	0	0	-



# 5. Serial Adder

